


```
endmodule
```

```
module counter (enable, clock, clear_b, q);
```

```
    input enable, clock, clear_b;
```

```
    output wire[7:0] q;
```

```
    tflipflop T0 (
```

```
        .t(enable),
```

```
        .clock(clock),
```

```
        .clear_b(clear_b),
```

```
        .q(q[0])
```

```
    );
```

```
    tflipflop T1 (
```

```
        .t(enable && (& q[0])),
```

```
        .clock(clock),
```

```
        .clear_b(clear_b),
```

```
        .q(q[1])
```

```
    );
```

```
    tflipflop T2 (
```

```
        .t(enable && (& q[1:0])),
```

```
        .clock(clock),
```

```
        .clear_b(clear_b),
```

```
        .q(q[2])
```

```
    );
```

```
    tflipflop T3 (
```

```
        .t(enable && (& q[2:0])),
```

```
        .clock(clock),
```

```
        .clear_b(clear_b),
```

```
        .q(q[3])
```

```
    );
```

```
    tflipflop T4 (
```

```
        .t(enable && (& q[3:0])),
```

```
        .clock(clock),
```

```
        .clear_b(clear_b),
```

```
.q(q[4])  
);
```

```
tflipflop T5 (  
  .t(enable && (& q[4:0])),  
  .clock(clock),  
  .clear_b(clear_b),  
  .q(q[5])  
);
```

```
tflipflop T6 (  
  .t(enable && (& q[5:0])),  
  .clock(clock),  
  .clear_b(clear_b),  
  .q(q[6])  
);
```

```
tflipflop T7 (  
  .t(enable && (& q[6:0])),  
  .clock(clock),  
  .clear_b(clear_b),  
  .q(q[7])  
);
```

```
endmodule
```

```
module tflipflop (t, clock, clear_b, q);
```

```
  input t, clock, clear_b;  
  output reg q;
```

```
  always @(posedge clock, negedge clear_b)  
  begin  
    if(~clear_b)  
      q <= 0;  
    else  
      q <= q ^ t;  
    end
```

```
endmodule
```

```

module sevenseg (Display, Data);
    input[3:0] Data;
    output[6:0] Display;

    assign Display[0] = ~Data[3] & ~Data[2] & ~Data[1] & Data[0] |
        ~Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        Data[3] & Data[2] & ~Data[1] & Data[0] |
        Data[3] & ~Data[2] & Data[1] & Data[0];

    assign Display[1] = ~Data[3] & Data[2] & ~Data[1] & Data[0] |
        Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        Data[3] & Data[1] & Data[0] |
        Data[2] & Data[1] & ~Data[0];

    assign Display[2] = Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        ~Data[3] & ~Data[2] & Data[1] & ~Data[0] |
        Data[3] & Data[2] & Data[1];

    assign Display[3] = ~Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        ~Data[2] & ~Data[1] & Data[0] |
        Data[2] & Data[1] & Data[0] |
        Data[3] & ~Data[2] & Data[1] & ~Data[0];

    assign Display[4] = ~Data[3] & Data[0] |
        ~Data[3] & Data[2] & ~Data[1] |
        ~Data[2] & ~Data[1] & Data[0];

    assign Display[5] = ~Data[3] & ~Data[2] & Data[0] |
        ~Data[3] & ~Data[2] & Data[1] |
        ~Data[3] & Data[1] & Data[0] |
        Data[3] & Data[2] & ~Data[1] & Data[0];

    assign Display[6] = ~Data[3] & ~Data[2] & ~Data[1] |
        ~Data[3] & Data[2] & Data[1] & Data[0] |
        Data[3] & Data[2] & ~Data[1] & ~Data[0];

Endmodule

```

VSIM CODE

Set the working dir, where all compiled Verilog goes.

```
vlib work
```

Compile all verilog modules in mux.v to working dir;

could also have multiple verilog files.

```
vlog -timescale 1ns/1ns main_counter.v
```

Load simulation using mux as the top level simulation module.

```
vsim main_counter
```

```
#SW[1] is enable      SW[0] clear_b
```

Log all signals and add some signals to waveform window.

```
log {/*}
```

add wave {/*} would add all items in top level simulation module.

```
add wave {/*}
```

```
#SW[1] is enable      SW[0] clear_b
```

Set input values using the force command, signal names need to be in {} brackets.

```
force {SW[0]} 0
```

```
run 10ns
```

```
force {SW[0]} 1
```

```
run 10ns
```

```
force {KEY[0]} 0 0, 1 10 -repeat 10
```

```
force {SW[1]} 1
```

```
run 10ns
```

```
run 10ns
```

```
run 10ns
```

```
run 10ns
```

```
run 10ns
```


```
run 10ns
```

```
run 10ns
```

```
run 10ns
```

```
run 10ns
```

VSIM SCREENSHOT

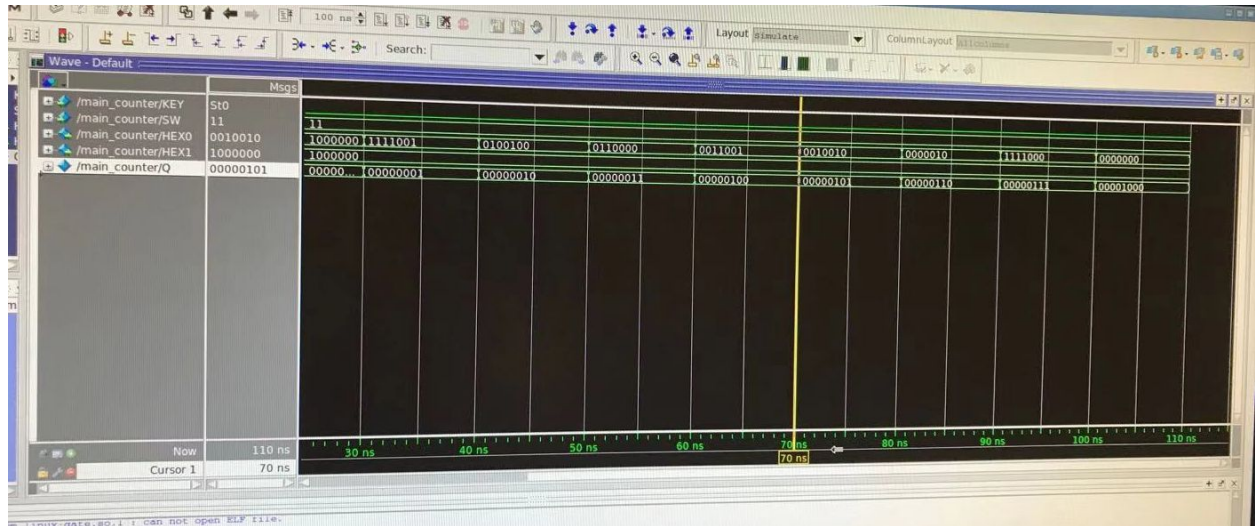

Questions


<1 percent

621.89MHz

There are four more counters in our implementation furthermore, there is two seven segment decoders connected to the output of the 8 bit counter.

PART 2

Schematic

 

Questions

Because you cannot reach F with 4 bits

If (q == 1001)

It will be so fast it will go from 0 to F instantly.

You will need 26 bits to count to 1 HZ from 50MHZ blocks.

VERILOG CODE

```
module zeroToF (SW, KEY, CLOCK_50, HEX0);
    input CLOCK_50;
        input [1:0] SW;
        input [1:0] KEY;
        input [6:0] HEX0;

    reg [28:0] period;
    wire [28:0] rateDividerOutput;
    wire counterEnable;
    wire [3:0] counterOut;

    always @(SW)
        begin
            case (SW[1:0])
                2'b00: period <= 1;
                2'b01: period <= 500000000;
                2'b10: period <= 1000000000;
                2'b11: period <= 2000000000;
                default: period <= 1;
            endcase
        end

    assign counterEnable = (rateDividerOutput == 0) ? 1 : 0;

    rateDivider rd1(
        .par_load(period),
        .clock(CLOCK_50),
        .reset_n(KEY[0]),
        .q(rateDividerOutput)
    );

    fourbitcounter fbc1(
        .enable(counterEnable),
        .clock(CLOCK_50),
        .reset_n(KEY[0]),
        .q(counterOut)
    );
endmodule
```

```

    sevenseg ss1(
        .Data(counterOut),
        .Display(HEX0)
    );
endmodule

```

```

module rateDivider (par_load, clock, reset_n, q);
    input [28:0] par_load;
    input clock;
    input reset_n;

    output reg[28:0] q;

    always @(posedge clock)
    begin
        if (reset_n == 1'b0)
            q <= par_load - 1'b1;
        else
            begin
                if (q == 0)
                    q <= par_load - 1'b1;
                else
                    q <= q - 1'b1;
            end
        end
    end
endmodule

```

```

module fourbitcounter (enable, clock, reset_n, q);

    input enable, clock, reset_n;
    output reg[3:0] q;

    always @(posedge clock)
    begin
        if (reset_n == 1'b0)
            q <= 0;
        else if (enable == 1)
            begin
                if (q==4'b1111)
                    q <= 0;
            end
        end
    end
endmodule

```



```

                else
                    q <= q + 1'b1;
                end
            end
        end

endmodule

module sevenseg (Display, Data);
    input[3:0] Data;
    output[6:0] Display;

    assign Display[0] = ~Data[3] & ~Data[2] & ~Data[1] & Data[0] |
        ~Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        Data[3] & Data[2] & ~Data[1] & Data[0] |
        Data[3] & ~Data[2] & Data[1] & Data[0];

    assign Display[1] = ~Data[3] & Data[2] & ~Data[1] & Data[0] |
        Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        Data[3] &          Data[1] & Data[0] |
        Data[2] & Data[1] & ~Data[0];

    assign Display[2] = Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        ~Data[3] & ~Data[2] & Data[1] & ~Data[0] |
        Data[3] & Data[2] & Data[1];

    assign Display[3] = ~Data[3] & Data[2] & ~Data[1] & ~Data[0] |
        ~Data[2] & ~Data[1] & Data[0] |
        Data[2] & Data[1] & Data[0] |
        Data[3] & ~Data[2] & Data[1] & ~Data[0];

    assign Display[4] = ~Data[3] &          Data[0] |
        ~Data[3] & Data[2] & ~Data[1]      |
        ~Data[2] & ~Data[1] & Data[0];

    assign Display[5] = ~Data[3] & ~Data[2]          & Data[0] |
        ~Data[3] & ~Data[2] & Data[1]      |
        ~Data[3] &          Data[1] & Data[0] |
        Data[3] & Data[2] & ~Data[1] & Data[0];

    assign Display[6] = ~Data[3] & ~Data[2] & ~Data[1]      |
        ~Data[3] & Data[2] & Data[1] & Data[0] |

```

```
Data[3] & Data[2] & ~Data[1] & ~Data[0];
```

```
endmodule
```

VSIM CODE

```
# Set the working dir, where all compiled Verilog goes.
```

```
vlib work
```

```
# Compile all verilog modules in mux.v to working dir;
```

```
# could also have multiple verilog files.
```

```
vlog -timescale 1ns/1ns lab5part2.v
```

```
# Load simulation using mux as the top level simulation module.
```

```
vsim zeroToF
```

```
#SW[1] is enable      SW[0] clear_b
```

```
# Log all signals and add some signals to waveform window.
```

```
log {/*}
```

```
# add wave {/*} would add all items in top level simulation module.
```

```
add wave {/*}
```

```
#SW[1]      SW[0]      reset = KEY[0](active low)
```

```
#test 1HZ case
```

```
# reset, set initial values
```

```
force {SW[0]} 0
```

```
force {SW[1]} 0
```

```
force {KEY[0]} 0
```

```
run 1ns
```

```
#go thru one cycle
```

```
force {CLOCK_50} 0
```

```
run 1ns
```

```
force {CLOCK_50} 1
```

```
run 1ns
```

```
# turn off reset
```

```
force {KEY[0]} 1
```

```
run 1ns
```

```
# clock speed
```

```
force {CLOCK_50} 0 0, 1 1 -repeat 2
```

```
force {SW[0]} 0
```


```
force {SW[1]} 0
```

```
run 10ns
```

```
run 10ns
```

```
run 10ns
run 10ns
run 10ns
run 10ns
```

VSIM SCREENSHOT

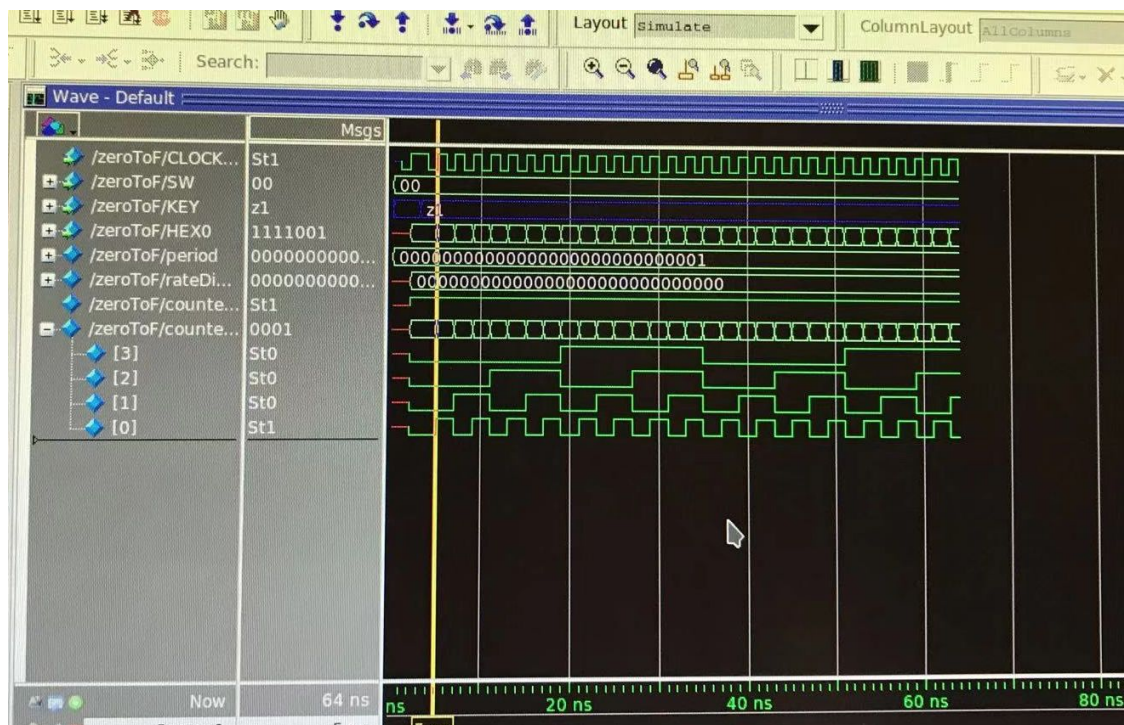

PART 3


TABLE

abcdef

S	1010100000000
T	1110000000000
U	1010111000000
V	1010101110000
W	1011101110000
X	1110101011100
Y	1110101110111
Z	1110111010100

13 bit width

SCHEMATIC

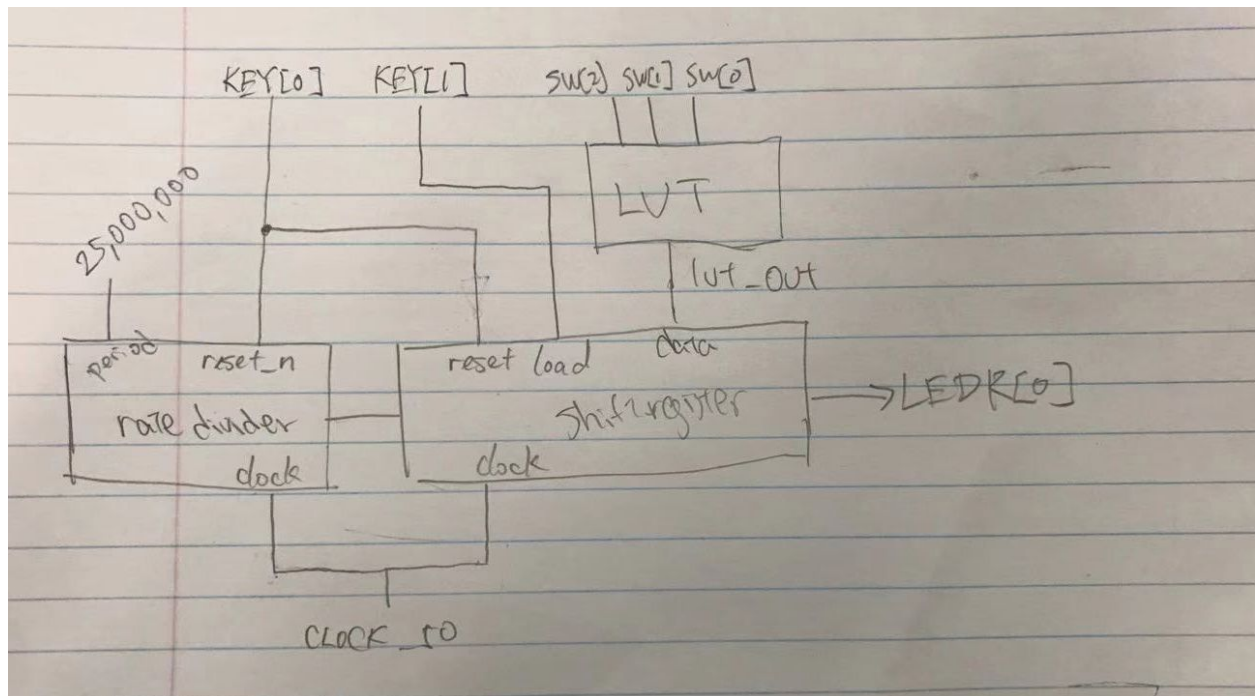

VERILOG CODE

```
module morse (KEY, SW, CLOCK_50, LEDR);

    input CLOCK_50;
    input [1:0] KEY;
    input [2:0] SW;

    output [1:0] LEDR;

    wire [28:0] period;
    wire [28:0] rateDividerOut;
    wire [15:0] lutOut;
    wire shiftEnable;

    assign period = 25000000;

    lut u0 (
        .letter(SW[2:0]),
        .morseCode(lutOut)
    );

    rateDivider rd1 (
        .clock(CLOCK_50),
        .period(period),
        .reset_n(KEY[0]),
        .q(rateDividerOut)
    );
    assign shiftEnable = (rateDividerOut == 0) ? 1 : 0;

    shifter s1 (
        .clock(CLOCK_50),
        .load(KEY[1]),
        .enable(shiftEnable),
        .reset(KEY[0]),
        .data(lutOut),
        .out(LEDR[0])
    );

endmodule
```

```

module lut(letter, morseCode);

    input [2:0] letter;
    output reg [15:0] morseCode;

    always @(*)
    begin
        case(letter)
            3'b000: morseCode = 16'b1010100000000000;
            3'b001: morseCode = 16'b1110000000000000;
            3'b010: morseCode = 16'b1010111000000000;
            3'b011: morseCode = 16'b1010101110000000;
            3'b100: morseCode = 16'b1011101110000000;
            3'b101: morseCode = 16'b1110101011100000;
            3'b110: morseCode = 16'b1110101110111000;
            3'b111: morseCode = 16'b1110111010100000;
            default: morseCode = 16'b0000000000000000;
        endcase
    end

endmodule

```

```

module rateDivider (clock, period, reset_n, out);

    input clock;
    input reset_n;
    input [28:0] period;

    output reg [28:0] out;

    always @(posedge clock, posedge reset_n)
    begin
        if (reset_n == 1'b0)
            out <= period - 1'b1;
        else
            begin
                if (out == 0)
                    out <= period - 1'b1;
                else
                    out <= out - 1'b1;
            end
        end
    end

```

end

endmodule

module shifter(enable, load, clock, reset, data, out);

input enable, load, clock, reset;

input [15:0] data;

reg [15:0] MCodeBit;

output out;

always @(posedge load, posedge clock, posedge reset)

begin

if (load)

MCodeBit = data;

else if (reset)

MCodeBit = 0;

else if (enable == 1'b1)

MCodeBit = MCodeBit << 1'b1;

end

assign out = MCodeBit[15];

endmodule