 


Ryan chang csc258 prelab3

Part 1

Schematic



1.

2.

VERILOG CODE

* rememebr that its called seven mux and idk if u can do line 3?

```
module mux(SW,LEDR);  
    input [9:0] SW;  
    output [1:0] LEDR;
```

```
    mux7to1 u0(  
        .Input(SW[6:0]),  
        .MuxSelect(SW[9:7]),  
        .m(LEDR[0])  
    );
```

```

endmodule

module mux7to1(Input, MuxSelect, m);
    input [6:0] Input;
    input [2:0] MuxSelect;
    output m;
    reg m;

    always @(*)
    begin
        case(MuxSelect)
            3'b000: m = Input[0];
            3'b001: m = Input[1];
            3'b010: m = Input[2];
            3'b011: m = Input[3];
            3'b100: m = Input[4];
            3'b101: m = Input[5];
            3'b110: m = Input[6];
            default: m = 1'b0;
        endcase
    end
endmodule

```

SIM CODE

Set the working dir, where all compiled Verilog goes.

vlib work

Compile all verilog modules in mux.v to working dir;

could also have multiple verilog files.

vlog -timescale 1ns/1ns mux7to1.v

Load simulation using mux as the top level simulation module.

vsim mux

Log all signals and add some signals to waveform window.

log {/*}

add wave {/*} would add all items in top level simulation module.

add wave {/*}

#the LEDR should all be 1 for all 70ns

```
#test input0
force {SW[0]} 1
force {SW[9]} 0
force {SW[8]} 0
force {SW[7]} 0
run 10ns
```

```
#test input1
force {SW[1]} 1
force {SW[9]} 0
force {SW[8]} 0
force {SW[7]} 1
run 10ns
```

```
#test input2
force {SW[2]} 1
force {SW[9]} 0
force {SW[8]} 1
force {SW[7]} 0
run 10ns
```

```
#test input3
force {SW[3]} 1
force {SW[9]} 0
force {SW[8]} 1
force {SW[7]} 1
run 10ns
```

```
#test input4
force {SW[4]} 1
force {SW[9]} 1
force {SW[8]} 0
force {SW[7]} 0
run 10ns
```

```
#test input5
force {SW[5]} 1
force {SW[9]} 1
force {SW[8]} 0
force {SW[7]} 1
run 10ns
```


```
#test input6
```

```

force {SW[6]} 1
force {SW[9]} 1
force {SW[8]} 1
force {SW[7]} 0
run 10ns


```

Sim screenshot

 

Part 2

Schematic

 

VERILOG CODE

```

module fourbitadder(SW,LEDR);
    input [9:0] SW;
    output [9:0] LEDR;
    wire w1, w2, w3;

    fullAdder fa1(
        .a(SW[0]),
        .b(SW[1]),
        .cin(SW[2]),
        .s(LEDR[0]),
        .cout(w1)
    );

    fullAdder fa2(
        .a(SW[3]),
        .b(SW[4]),
        .cin(w1),
        .s(LEDR[1]),
        .cout(w2)
    );

```

```

);

fullAdder fa3(
    .a(SW[5]),
    .b(SW[6]),
    .cin(w2),
    .s(LED[2]),
    .cout(w3)
);

fullAdder fa4(
    .a(SW[7]),
    .b(SW[8]),
    .cin(w3),
    .s(LED[3]),
    .cout(LED[4])
);

endmodule

```

```

module fullAdder(a, b, cin, s, cout);
    input a;
    input b;
    input cin;
    output s;
    output cout;

    assign cout = a & b | a & cin | b & cin;
    assign s = a ^ b ^ cin;
endmodule

```

Vsim code

```

# Set the working dir, where all compiled Verilog goes.
vlib work

```

```

# Compile all verilog modules in mux.v to working dir;
# could also have multiple verilog files.

```

```
vlog -timescale 1ns/1ns fourbitadder.v
```

```
# Load simulation using mux as the top level simulation module.
```

```
vsim fourbitadder
```

```
# Log all signals and add some signals to waveform window.
```

```
log {/*}
```

```
# add wave {/*} would add all items in top level simulation module.
```

```
add wave {/*}
```

```
#test case 1: adding 2#1111 + 2#1111 = 2#11111 also 10#15 + 10#15 = 10#30
```

```
force {SW[0]} 1
```

```
force {SW[1]} 1
```

```
force {SW[2]} 0
```

```
force {SW[3]} 1
```

```
force {SW[4]} 1
```

```
force {SW[5]} 1
```

```
force {SW[6]} 1
```

```
force {SW[7]} 1
```

```
force {SW[8]} 1
```

```
run 10ns
```

```
#test case 2: adding 2#0001 + 2#0001 = 2#0010 also 10#1 + 10#1 = 10#2
```

```
force {SW[0]} 1
```

```
force {SW[1]} 1
```

```
force {SW[2]} 0
```

```
force {SW[3]} 0
```

```
force {SW[4]} 0
```

```
force {SW[5]} 0
```


```
force {SW[6]} 0
```

```
force {SW[7]} 0
```


```
force {SW[8]} 0
```

```
run 10ns
```

SIM SCREENSHOT

 

Part 3
Schematic

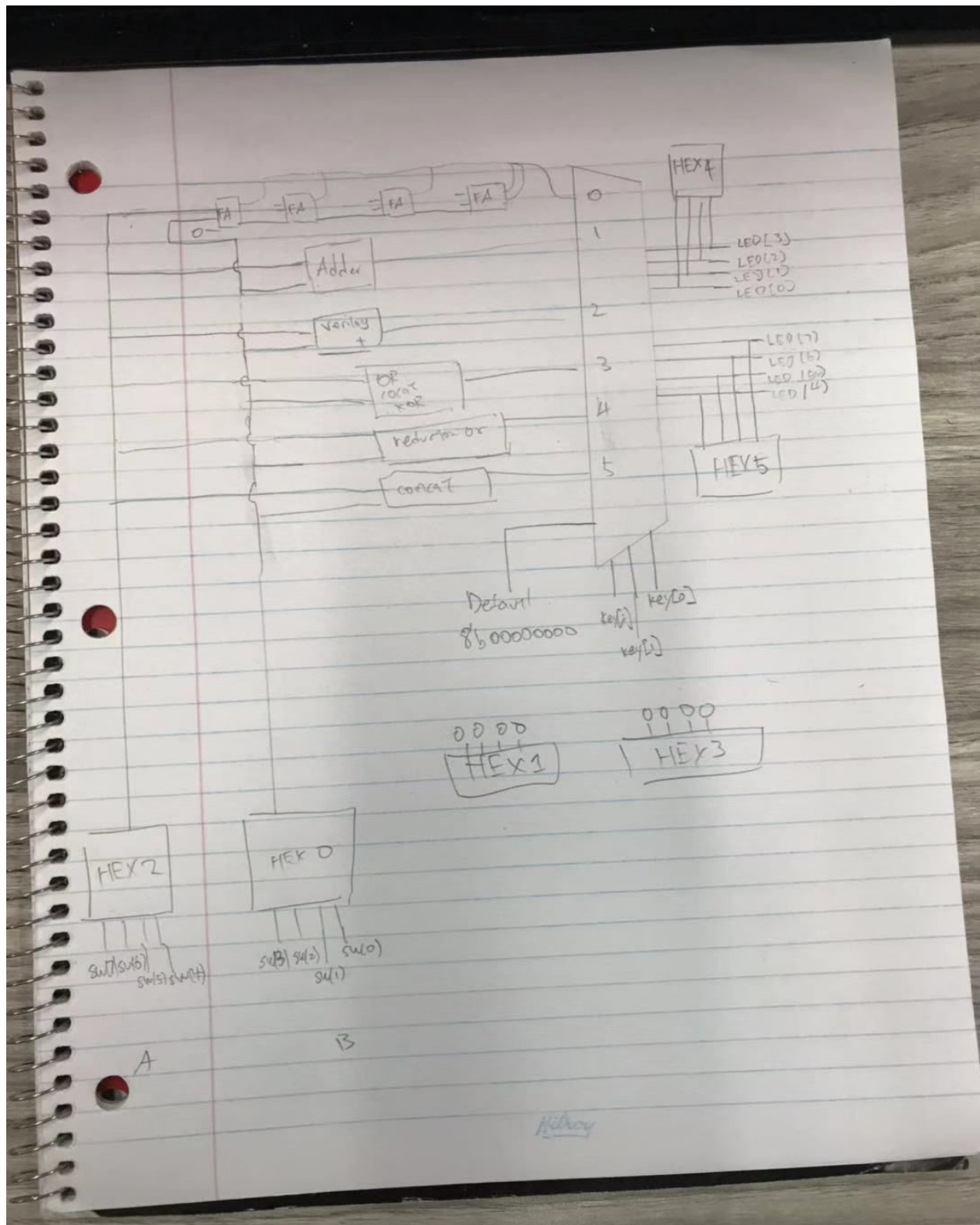

Verilog Code

```
module mainalu(SW, KEY, LEDR, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5);
    input [7:0] SW;
    input [2:0] KEY;
    output [7:0] LEDR;

    output[6:0] HEX0;
    output[6:0] HEX1;
    output[6:0] HEX2;
    output[6:0] HEX3;
    output[6:0] HEX4;
    output[6:0] HEX5;

    wire[7:0] Case0;
    wire[7:0] Case1;
    wire[7:0] Case2;
    wire[7:0] Case3;
    wire[7:0] Case4;
    wire[7:0] Case5;

    reg[7:0] Out;

    fourbitadder fba1(
        .A(SW[7:4]),
        .B(4'b0001),
        .Cin(1'b0),
        .Sum(Case0[7:0])
    );

    fourbitadder fba1(
        .A(SW[7:4]),
        .B(SW[3:0]),
        .Cin(1'b0),
        .Sum(Case1[7:0])
    );

    verisum v1(
        .A(SW[7:4]),
        .B(SW[3:0]),
        .Sum(Case2[7:0])
    );
```

```

veriXOR v2(
    .A(SW[7:4]),
    .B(SW[3:0]),
    .Sum(Case3[7:0])
);

```

```

orplusredor o3(
    .A(SW[7:4]),
    .B(SW[3:0]),
    .Sum(Case4[7:0])
);

```

```

concat c1(
    .A(SW[7:4]),
    .B(SW[3:0]),
    .Sum(Case5[7:0])
);

```

```

always @(*)
begin
    case (KEY[2:0])
        3'b000: Out = Case0;
        3'b001: Out = Case1;
        3'b010: Out = Case2;
        3'b011: Out = Case3;
        3'b100: Out = Case4;
        3'b101: Out = Case5;
        default: Out = 8'b000000000;
    endcase
end

```

```

assign LEDR = Out;

```

```

sevenseg u6 (
    .Data(SW[3:0]),
    .Display(HEX0[6:0])

);

```

```

sevenseg u7 (
    .Data(SW[7:4]),

```

```
.Display(HEX2[6:0])  
);
```

```
sevenseg u8 (  
.Data(Out[3:0]),  
.Display(HEX4[6:0])  
);
```

```
sevenseg u9 (  
.Data(Out[7:4]),  
.Display(HEX5[6:0])  
  
);
```

```
assign HEX1[6:0] = 7'b00000000;  
assign HEX3[6:0] = 7'b00000000;
```

```
endmodule
```

```
module fourbitadder(A, B, Cin, Sum);  
    input [3:0] A, B;  
    input Cin;  
    output [7:0] Sum;  
    wire w1, w2, w3;
```

```
    fullAdder fa1(  
        .a(A[0]),  
        .b(B[0]),  
        .cin(Cin),  
        .s(Sum[0]),  
        .cout(w1)  
    );
```

```
    fullAdder fa2(  
        .a(A[1]),  
        .b(B[1]),  
        .cin(w1),  
        .s(Sum[1]),  
        .cout(w2)  
    );
```

```
    fullAdder fa3(  
    .a(A[2]),  
    .b(B[2]),  
    .cin(w2),  
    .s(Sum[2]),  
    .cout(w3)  
    );
```

```
    fullAdder fa4(  
    .a(A[3]),  
    .b(B[3]),  
    .cin(w3),  
    .s(Sum[3]),  
    .cout(Sum[4])  
    );  
    assign Sum[7:5] = 3'b000;
```

```
endmodule
```

```
module fullAdder(a, b, cin, s, cout);  
    input a;  
    input b;  
    input cin;  
    output s;  
    output cout;  
  
    assign cout = a & b | a & cin | b & cin;  
    assign s = a ^ b ^ cin;  
endmodule
```

```
module verisum(A, B, Result);  
    input[3:0] A;  
    input[3:0] B;  
    output[7:0] Result;  
  
    assign Result[3:0] = A + B;  
    assign Result[7:4] = 4'b0000;
```

```
endmodule
```

```

module orplusredor(A, B, Result);
    input[3:0] A;
    input[3:0] B;
    output[7:0] Result;

    assign Result[0] = | {A,B};
    assign Result[7:1] = 7'b00000000;

```

```

endmodule

```

```

module concant(A, B, Result);
    input[3:0] A;
    input[3:0] B;
    output[7:0] Result;

    assign Result[7:0] = {A, B};

```

```

endmodule

```

```

module sevenseg (Display, Data);

    input[3:0] Data;

    output[6:0] Display;

    assign Display[0] = ~Data[3] & ~Data[2] & ~Data[1] & Data[0] | ~Data[3] & Data[2] &
~Data[1] & ~Data[0] | Data[3] & Data[2] & ~Data[1] & Data[0] | Data[3] & ~Data[2] & Data[1] &
Data[0];

    assign Display[1] = ~Data[3] & Data[2] & ~Data[1] & Data[0] | Data[3] & Data[2] &
~Data[1] & ~Data[0] | Data[3] & Data[1] & Data[0] | Data[2] & Data[1] & ~Data[0];

    assign Display[2] = Data[3] & Data[2] & ~Data[1] & ~Data[0] | ~Data[3] & ~Data[2] &
Data[1] & ~Data[0] | Data[3] & Data[2] & Data[1];

    assign Display[3] = ~Data[3] & Data[2] & ~Data[1] & ~Data[0] | ~Data[2] & ~Data[1] &
Data[0] | Data[2] & Data[1] & Data[0] | Data[3] & ~Data[2] & Data[1] & ~Data[0];

```

```
    assign Display[4] = ~Data[3] & Data[0] | ~Data[3] & Data[2] & ~Data[1] | ~Data[2] &
~Data[1] & Data[0];
```

```
    assign Display[5] = ~Data[3] & ~Data[2] & Data[0] | ~Data[3] & ~Data[2] & Data[1]
| ~Data[3] & Data[1] & Data[0] | Data[3] & Data[2] & ~Data[1] & Data[0];
```

```
    assign Display[6] = ~Data[3] & ~Data[2] & ~Data[1] | ~Data[3] & Data[2] & Data[1] &
Data[0] | Data[3] & Data[2] & ~Data[1] & ~Data[0];
```

```
endmodule
```